


# Magnitude Comparator

**Aim:** To perform magnitude comparator on the breadboard

## Components:

Component List			 Download CSV
Name	Quantity	Component	
P1	1	5, 5 Power Supply	
S1 S2 S3 S4	4	Slideswitch	
D1 D2 D3 D4 D5	5	Red LED	
R1 R2 R3 R4 R5	5	1 kΩ Resistor	
U1	1	Quad XOR gate	
U2	1	Hex Inverter	
U3	1	Quad AND gate	
U4	1	Quad OR gate	

## Procedure:

### Step 1: Understand the Concept

A 4-bit magnitude comparator compares two 4-bit binary numbers (A and B) and provides three outputs:

- $A > B$
- $A < B$
- $A = B$

### Step 2: Log in to Tinker cad

1. Go to the Tinker cad website and log in to your account.
2. Open the "Circuits" workspace from the dashboard.

### Step 3: Create a New Circuit

1. Click on "Create new Circuit."
2. Name your circuit project, for example, "4-bit Magnitude Comparator."

### Step 4: Add Components

1. **Breadboard:** Add a breadboard to organize your circuit neatly.
2. **Logic Gates:** Add the necessary logic gates (AND, OR, NOT, XOR) from the component's library.
3. **Switches:** Add 8 switches (4 for each binary number A and B).
4. **LEDs:** Add 3 LEDs to display the results ( $A > B$ ,  $A < B$ ,  $A = B$ ).
5. **Resistors:** Add resistors for the LEDs (typically 220 ohms).

6. **Wires:** Use wires to connect components.

## Step 5: Design the Comparator Circuit

### Step 5.1: Comparator Logic

The 4-bit magnitude comparator can be implemented using combinational logic circuits. The equations for the outputs are:

- $A=B$ : The bits of A are equal to the bits of B.
- $A>B$ : The most significant bit of A is greater than the most significant bit of B, or if the bits are equal, the next significant bit is compared, and so on.
- $A<B$ : The most significant bit of A is less than the most significant bit of B, or if the bits are equal, the next significant bit is compared, and so on.

### Step 5.2: Equality Comparison ( $A = B$ )

1. Use XNOR gates to compare each bit of A and B.
2. Combine the outputs of the XNOR gates using an AND gate to get the final  $A=B$  output.

### Step 5.3: Greater Than Comparison ( $A > B$ )

1. Use a combination of AND, OR, and NOT gates to compare the bits.
2. Start from the most significant bit and move to the least significant bit. Use logic to check if A is greater than B at any bit position while all more significant bits are equal.

### Step 5.4: Less Than Comparison ( $A < B$ )

1. Similar to the greater than comparison, but check if B is greater than A.

## Step 6: Connect Components

1. **Switches to Logic Gates:** Connect the switches representing A and B to the respective inputs of the XNOR, AND, OR, and NOT gates.
2. **Logic Gates to LEDs:** Connect the outputs of the logic gates to the LEDs to display the results.
3. **Power and Ground:** Ensure all components are connected to power (Vcc) and ground (GND).

## Step 7: Simulation



1. After connecting all components, start the simulation.
2. Toggle the switches to provide different 4-bit values for A and B.
3. Observe the LEDs to check if the circuit correctly indicates  $A > B$ ,  $A < B$ , or  $A = B$ .


## Step 8: Troubleshooting

If the circuit is not working as expected:

1. Check all connections to ensure they are correct.
2. Verify the logic gates' inputs and outputs.
3. Make sure there are no short circuits or loose connections.

## Schematic Circuit Diagram:

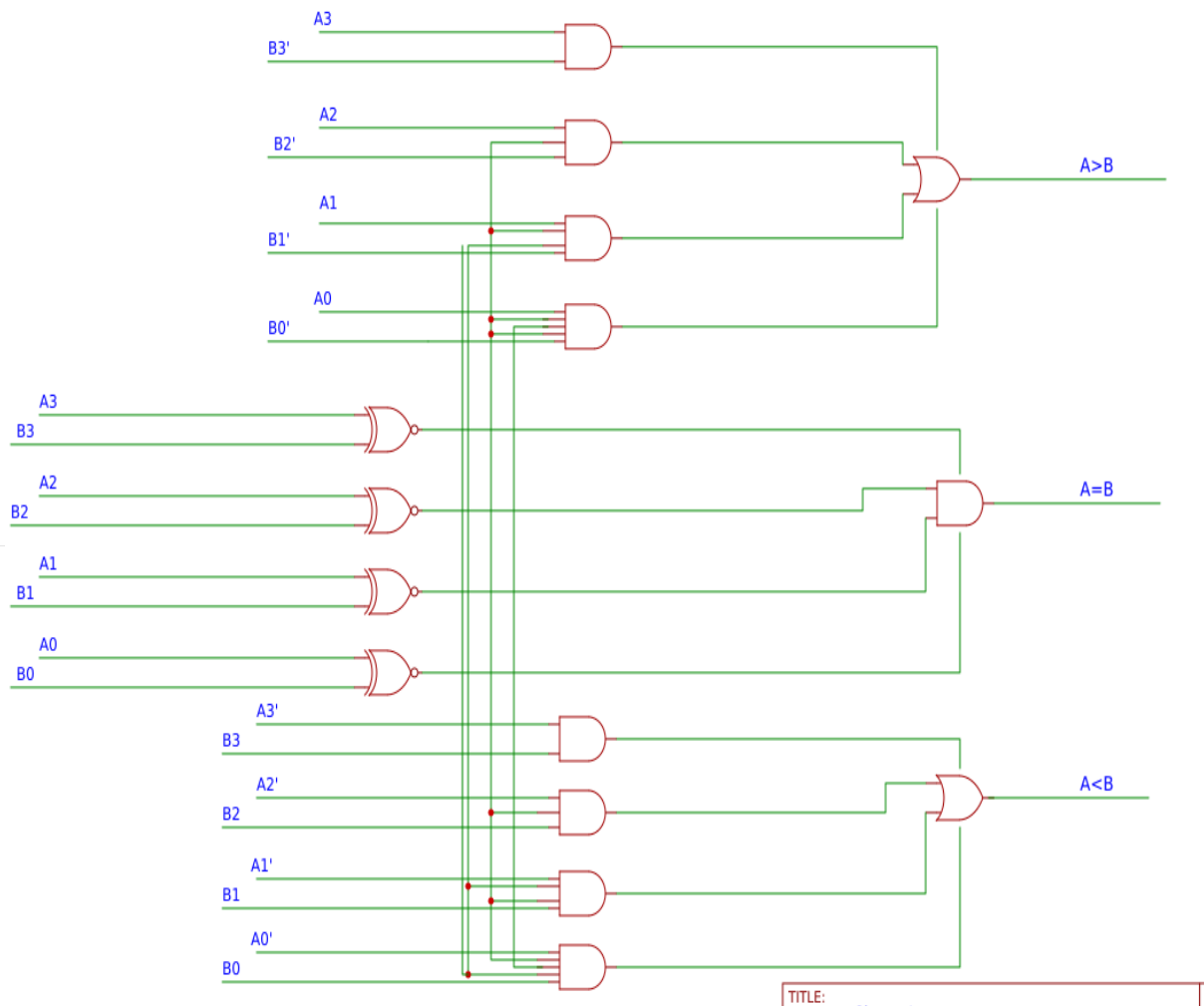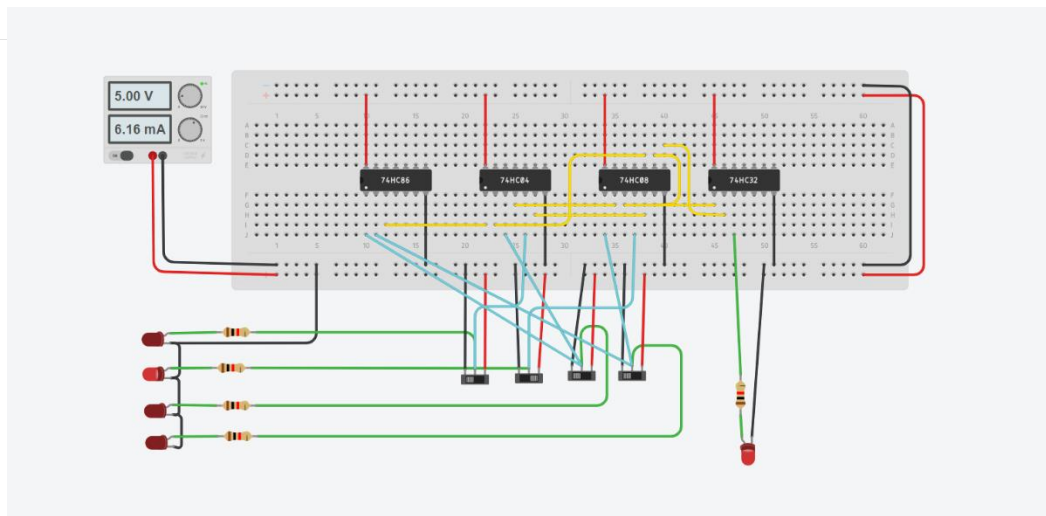

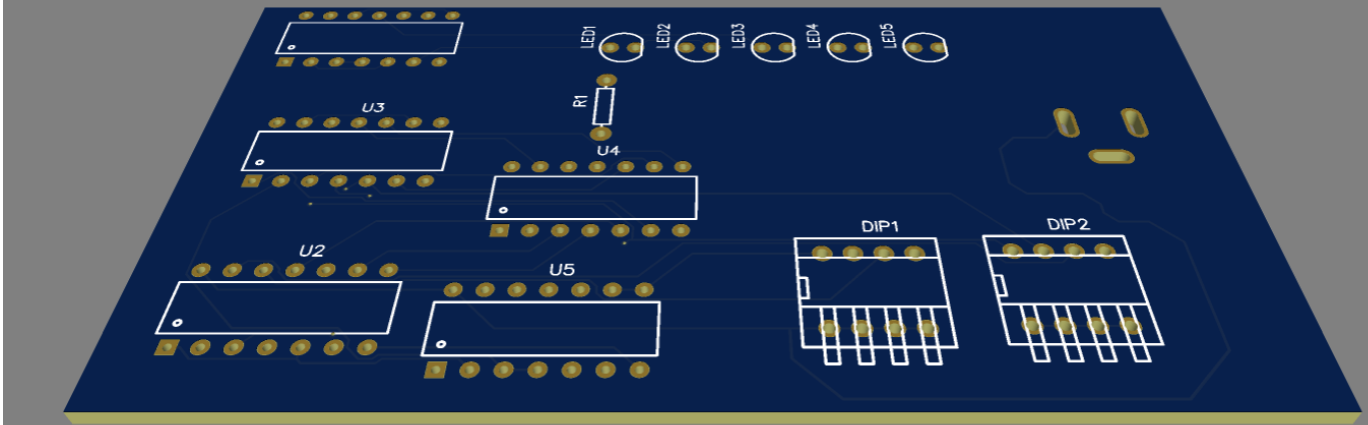

## **Result:**

Setting up and programming a magnitude comparator with an Arduino is a straightforward and rewarding project that enhances the understanding of hardware and software integration.

---

TAMMALI KARTHIK: BU21EECE0100164

MARIA PUNYA: BU21EECE0100309

ALLI GOPI: BU21EECE0100161

---